
 


Valve High Voltage Supply
Hybrid Boost Converter/Voltage Multiplier
+180V, 30mA @ 800kHz

Input power enters from a center-positive DC barrel jack, and is gated by an LTC360 input monitor and two series N-channel MOSFETs. Input voltage is a nominal 24V with a 22V undervoltage lockout and 26V overvoltage lockout. Input voltage presence is sensed by two signals sent to the microcontroller. The input power is fused at 3 Amps and the 24V monitored output voltage is the common voltage to all power converts, VCOM.

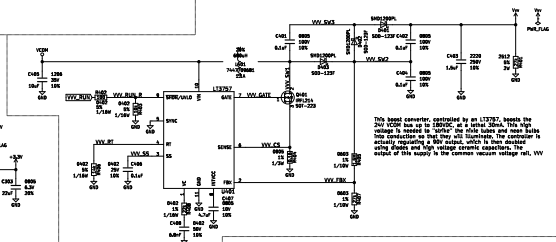


Common Voltage VCOM is switched by an LT3973, a wide input voltage buck converter with an integrated switch. This buck converter operates at a frequency of 2.3MHz and supplies the main logic voltage rail, VDD/VCC depending on logic technology. At 300mA, it has a power good signal (VCC_PS000) that notifies the microcontroller that the logic rail is up and running when input power is restored.




This boost converter, controlled by an LT3757, boosts the 24V VCOM bus up to 180VDC, at a lethal 30mA. This high voltage is needed to "strike" the nixie tubes and neon bulbs into conduction so that they will illuminate. The controller is actually regulating a 92V output, which is then doubled using diodes and high voltage ceramic capacitors. The output of this supply is the common vacuum voltage rail, VV


VVV PGOOD Window Comparator

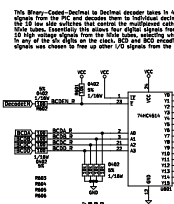


This Binary-Coded-Decimal to Decimal decoder takes in 4 signals from the PIC and decodes them to individual decimal digits. The 10 low side switches that control the multiplexed cathode tubes. Essentially this allows four digital signals from 10 high voltage signals from the tube tubes, selecting which in any of the six digits on the clock, BCD and BCD encoded signals was chosen to free up other I/O signals from the

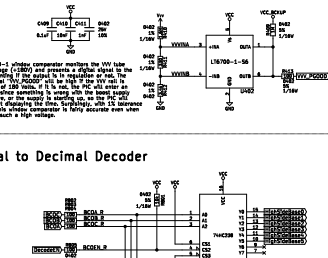

Time Set Pushbuttons

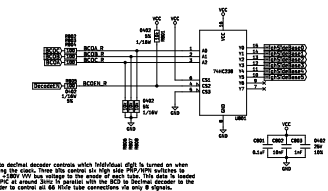


High Side BJT Switches

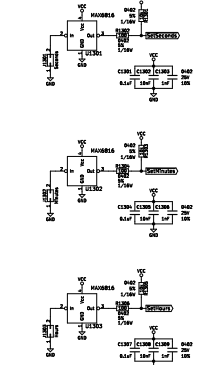


A fourth pushbutton is used to turn the clock display on and off. The PIC simply toggles the state of the high voltage VHV rail when it notices this button pressed. A three input AND gate switches an LED on when three important voltage rails have their power good flags set, showing that the voltage rails are in regulation when sampling the clock. These LEDs are switched by the PIC to show the DCS 3142 (nonimaging) signal if the clock is in an "enable" state, or if the clock is in an "S" state. Finally, a jumper sets whether or not the clock displays 24 hour or 12 hour time.


Other Functionality

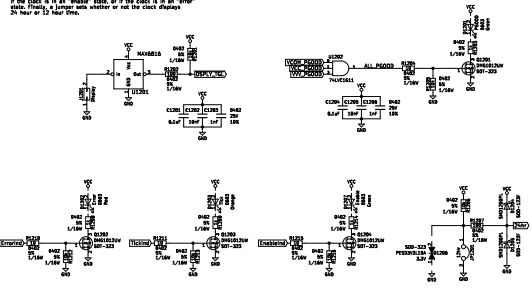

Colon Switches and Drivers

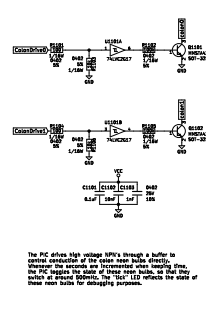

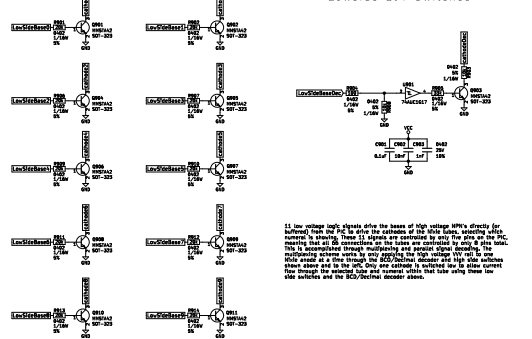
Downloaded from ascelibrary.org by New York University on 06/01/15. Copyright ASCE, For All Rights Reserved, No part of this document may be reproduced without written permission from ASCE.




11 low voltage logic signals drive the bases of high voltage NPN's directly (or buffered) from the PIC to drive the cathodes of the Mide tubes, selecting which numeral is showing. These 11 signals are controlled by only five pins on the PIC, resulting in all six connections on the tubes controlled by only 5 pins total. This is accomplished through multiplexing of the parallel signal decoding. The multiplexing scheme works by only applying the high voltage VV rail to one Mide anode at a time through the BCD/decimal decoder and high side switches shown above and to the left. Only one cathode is switched low to allow current flow through the selected tube and numeral within that tube using these low side switches and the BCD/decimal decoder above.

Display PCB

An external PCB holds all of the display elements for the clock, including the IN-14 tube tubes and two neon bulbs as separate units. It merges the connections for all cathodes together and keeps all the anodes separate for multiplexing, since the tubes are a common cathode design. A condenser sensing safety feature is also implemented with the multiplexing on the IN-14 tubes. The control headers at the rear of the board line up perfectly with the control board beneath to allow the two to seamlessly integrate. The IN-14 tube tubes included on the board were most likely manufactured in Russia sometime between the 1980's and 1990's, and are not produced anymore, meaning the kits on each board are getting increasingly rare and harder to find.

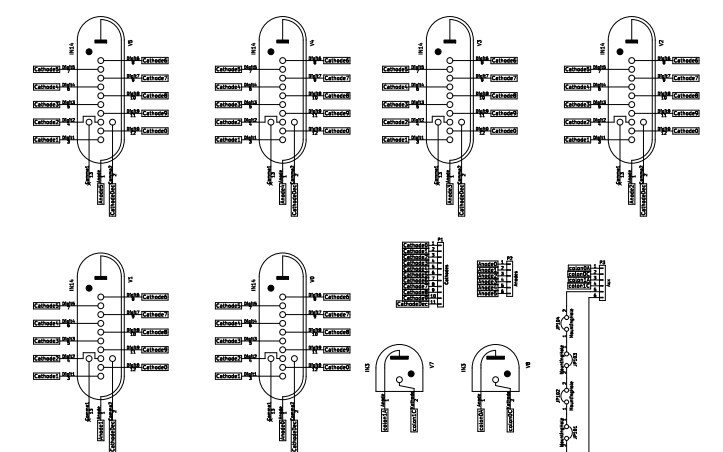

External Connections To Display PCB

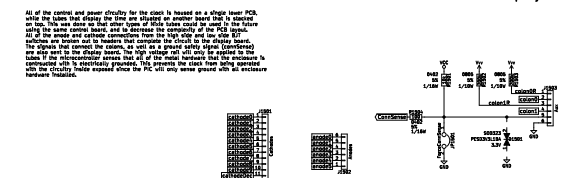

Other

- [illegible]

- 268 Parts
- 16 Integrated Circuits
- 1 Crystal Resonator
- 129 Resistors
- 30 Discrete Transistors
- 3 Inductors
- 13 Diodes
- 48 Capacitors
- BOM Price of \$160 Without tubes, PCBs, or Enclosure

[illegible]

Drew Haelman
Sheet 1 /
File: Nixie Clock.sch
Title: Nixie Clock Schematic Poster